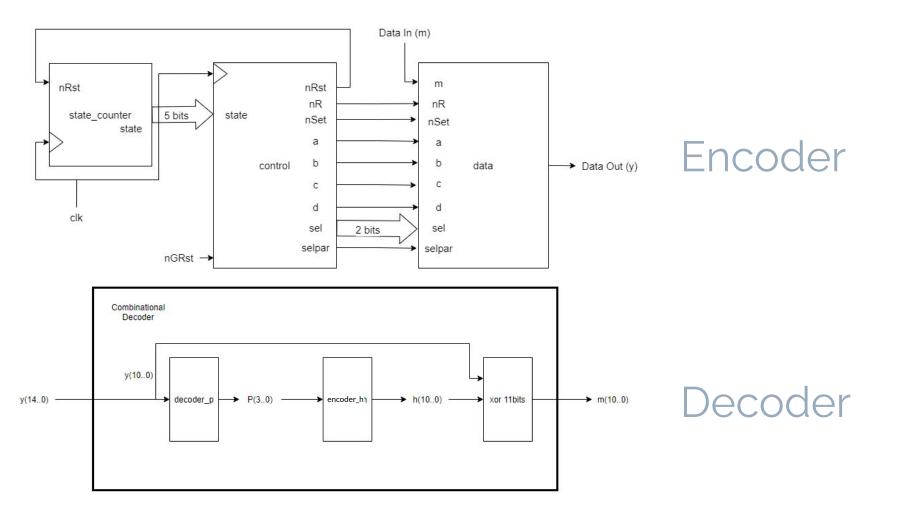


Assignment 1 – Hamming codes


Arquiteturas de Alto Desempenho

Work done by:

- -Lúcia Sousa 93086
- -Rodrigo Martins 93264 Gr5 TP2



Encoder Control Path

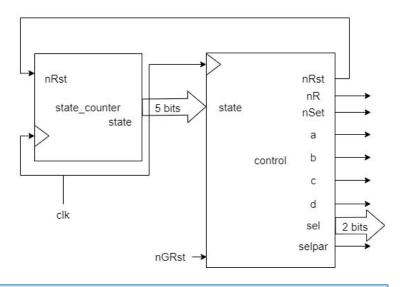

16 OR gates 57 AND gates



16 OR gates 37 AND gates

C4	C3	C2	C1	CO	nR	а	b	С	d	Sel1	Sel0	Selpar	nSet	nRst
0	0	0	0	0	1	1	1	0	0	0	0	0	1	1
0	0	0	0	1	1	1	0	1	0	0	0	0	1	1
0	0	0	1	0	1	1	0	0	1	0	0	0	1	1
0	0	0	1	1	1	0	1	1	0	0	0	0	1	1
0	0	1	0	0	1	0	1	0	1	0	0	0	1	1
0	0	1	0	1	1	0	0	1	1	0	0	0	1	1
0	0	1	1	0	1	1	1	1	0	0	0	0	1	1
0	0	1	1	1	1	1	1	0	1	0	0	0	1	1
0	1	0	0	0	1	1	0	1	1	0	0	0	1	1
0	1	0	0	1	1	0	1	1	1	0	0	0	1	1
0	1	0	1	0	1	1	1	1	1	0	0	0	1	1
0	1	0	1	1	1	0	0	0	0	0	0	1	1	1
0	1	1	0	0	1	0	0	0	0	0	1	1	1	1
0	1	1	0	1	1	0	0	0	0	1	0	1	1	1
0	1	1	1	0	1	0	0	0	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0	0	0	1	1
1	0	0	0	0	0	0	0	0	0	0	0	0	1	0

 $nR = \overline{C4}$

 $a = \overline{C4}.\overline{C2}.\overline{C0} + \overline{C3}.C2.C1 + \overline{C4}.\overline{C3}.\overline{C2}.\overline{C1}$

 $b = \overline{C3}.C1.C0 + \overline{C3}.C2.\overline{C0} + \overline{C4}.\overline{C3}.\overline{C1}.\overline{C0} + C3.\overline{C2}.\overline{C1}.C0 + C3.\overline{C2}.\overline{C1}.C0$

 $c = \overline{C3}.\overline{C2}.C0 + \overline{C3}.\overline{C1}.C0 + \overline{C2}.\overline{C1}.C0 + C3.\overline{C2}.\overline{C0} + \overline{C3}.C2.C1.\overline{C0}$

 $d = \overline{C2.C1.\overline{C0}} + \overline{C3.C2.\overline{C1}} + \overline{C3.C2.C0} + C3.\overline{C2.\overline{C1}}$


Sel1 = $C3.C2.\overline{C1}.C0 + C3.C2.C1.\overline{C0}$

Sel0 = $\overline{C4}$.C3.C2. $\overline{C0}$

Selpar = $\overline{C4}$.C3.C2. $\overline{C1}$ + $\overline{C4}$.C3.C2. $\overline{C0}$ + C3. $\overline{C2}$.C1.C0

 $nRst = \overline{C4}$


Encoder Data Path

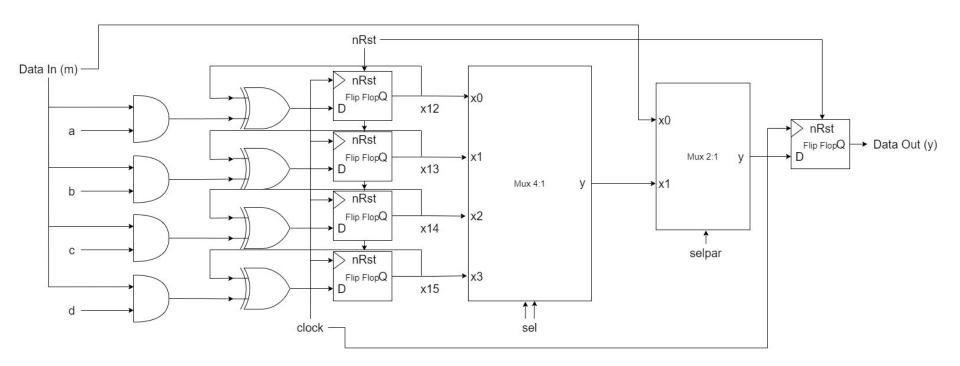

Decoder

decoder_p encoder_h decoder_h →h10 s7 s5) P3 s4) y10 -y13 -P2 P1 s3) P0 s2) s1 s0 y7 -y14 -→ h0 p4 y5 -22 XOR gates 19 AND gates 3 delays 2 delays

xor_11_bits

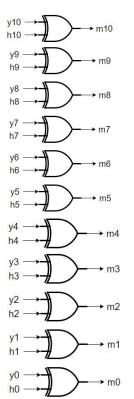

11 XOR gates

Truth Table encoder_h

H0 = 50.54
H1 = S1.S5
H2 = S2.S5
H3 = S1.S6
H4 = S2.S6
H5 = S3.S7
H6 = S1.S4
H7 = S2.S4
H8 = S3.S5

U0 - C0 C4


H9 = S3.S6

H10 = S3.S4

Р3	P2	P1	PO	H10	Н9	H8	H7	Н6	H5	H4	Н3	H2	H1	HO
0	0	1	1	0	0	0	0	0	0	0	0	0	0	1
0	1	0	1	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	0	1	0	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0

Conclusions

Encoder

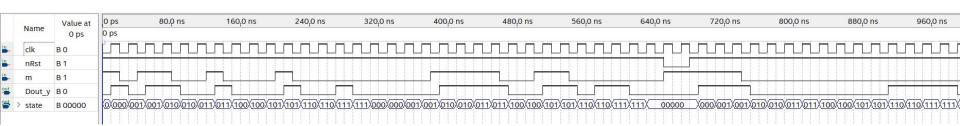

Decoder

